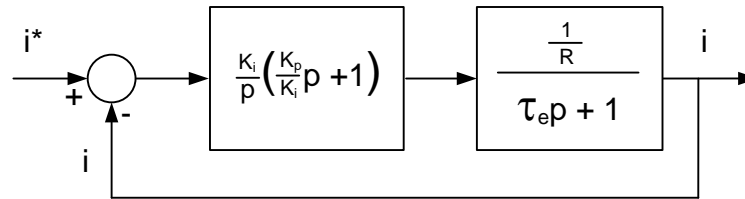


Recap of Current Loop Controls:




Current Regulation of DC Drive (with rotor locked)

Use Proportional plus Integral (PI) Control

$$G_c = K_p + \frac{K_i}{p} = \frac{K_i}{p} \left(\frac{K_p}{K_i} p + 1 \right) = \frac{K_p \left(p + \frac{K_i}{K_p} \right)}{p}$$

With $\tau_c = \tau_e$:

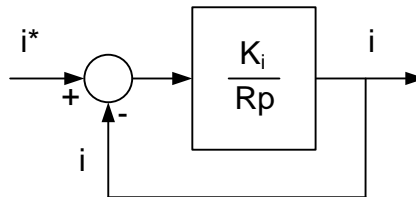

Current Regulation of DC Drive (with Back EMF Decoupled) and Pole/Zero Cancellation

$$\frac{I(p)}{I^*(p)} = \frac{K_i}{R_a p + K_i} \quad \text{why choose } K_i = 2\pi f_{desired} R_a?$$

$$\left| \frac{I(j\omega)}{I^*(j\omega)} \right| = \left| \frac{K_i}{R_a(j\omega) + K_i} \right| = \quad \angle \frac{I(j\omega)}{I^*(j\omega)} = 0^\circ - \tan^{-1} \left(\frac{R_a \omega}{K_i} \right)$$



If $R_a \omega = K_i$

Then


$$\left| \frac{I(j\omega)}{I^*(j\omega)} \right| =$$

EE 560 – Electric Machines and Drives

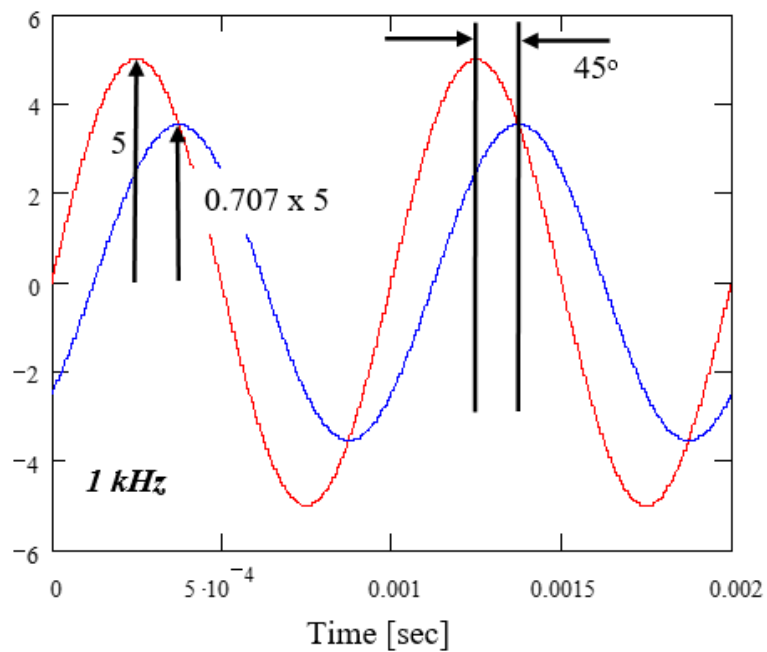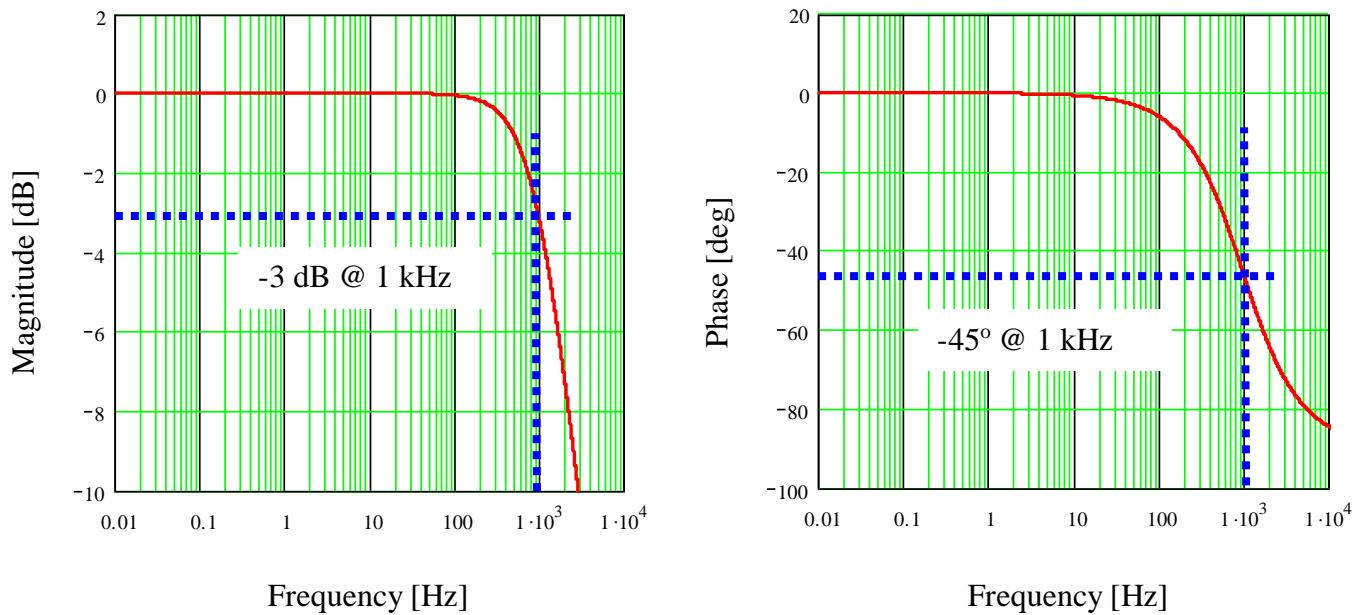Prof. N.J. Nagel, Autumn 2020 – Lecture 4



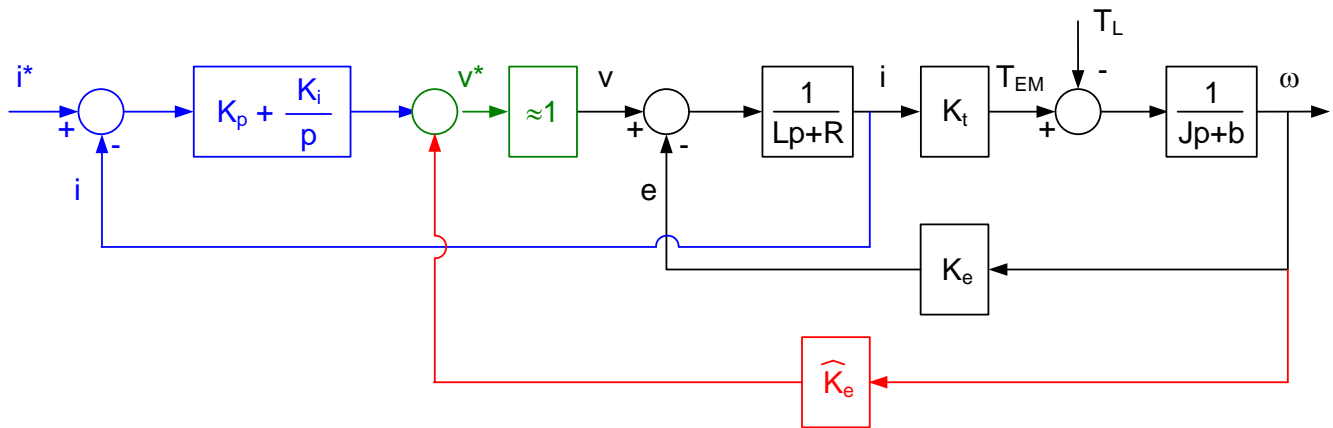
Note: By using Back EMF decoupling, the desired bandwidth can be achieved at non-zero speed conditions as well so long as the armature voltage is not saturated.



DC Motor PI Current Regulator with Back EMF Decoupling

Introduction to AC Induction Machines:

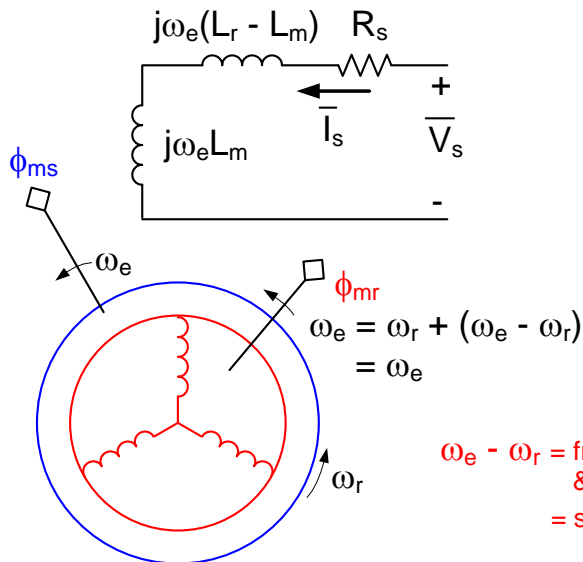Basic Theory of Squirrel Cage Induction Machines:




ω_e = excitation frequency

ω_r = rotor electrical speed

$$\omega_{em} = \frac{\omega_e}{P/2}$$

$$\omega_{rm} = \frac{\omega_r}{P/2}$$

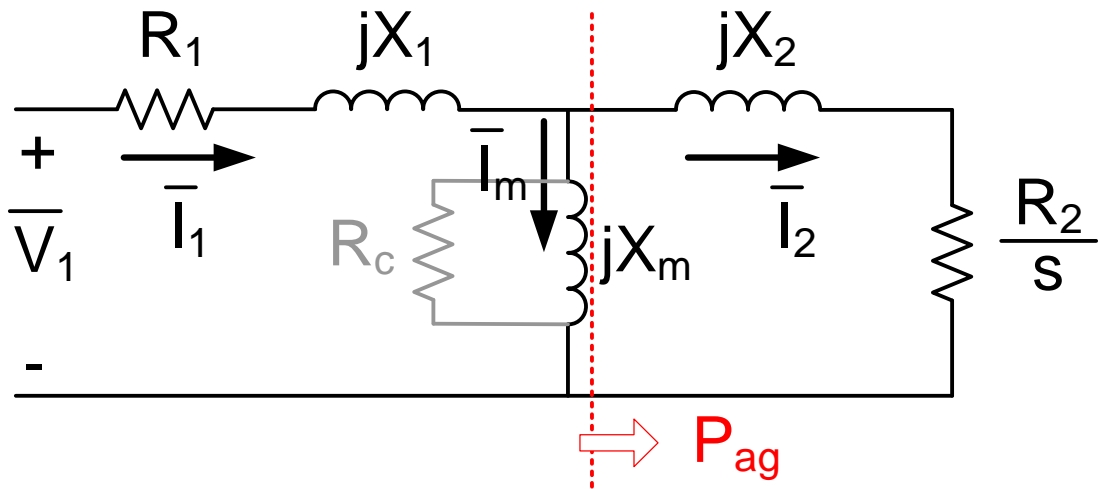Conventional Per Phase Equivalent Circuit:



Per Phase Equivalent Schematic of Induction Motor Reflected to Stator

Airgap Power:

$$P_{ag} = \frac{3I_2^2 R_2}{s} \rightarrow$$

Rotor Loss =

$$P_{out} = \frac{3I_2^2 R_2}{s} (1 - s) =$$

A good (efficient) induction motor must run with low slip.


Electromagnetic Torque:

$$T_{em} = \frac{P_{out}}{\omega_{rm}} =$$

$$T_{em} = \frac{3P}{2} \frac{I_2^2 R_2}{s \omega_e}$$

EE 560 – Electric Machines and Drives

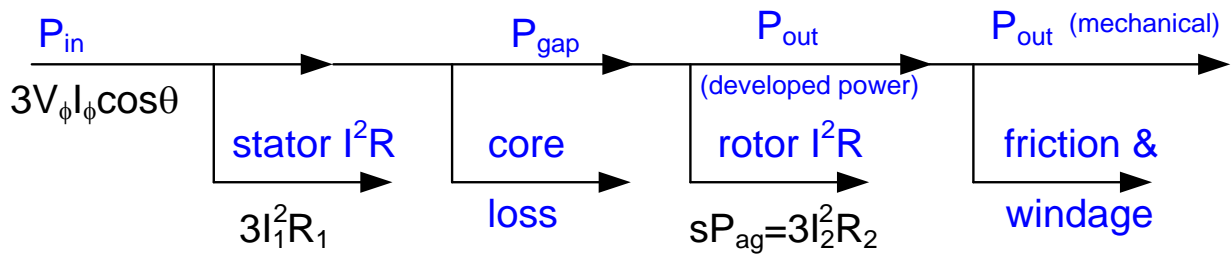Prof. N.J. Nagel, Autumn 2020 – Lecture 4



Power Flow in an Induction Motor

For a “good” motor

for sure:

$$R_1 \rightarrow$$


$$X_m \rightarrow$$

probably:

$$R_2 \rightarrow$$

$$X_1, X_2 \rightarrow$$

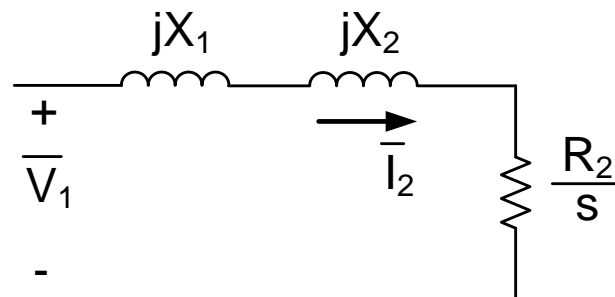Max P_{ag} (assuming small R_1 large X_m):




Per Phase Equivalent Schematic of Induction Assuming Small R_1 and Large X_m

Max P_{ag} when:

$$\frac{R_2}{s_{mt}} = X_1 + X_2$$


$$s_{mt} = \frac{R_2}{X_1 + X_2}$$
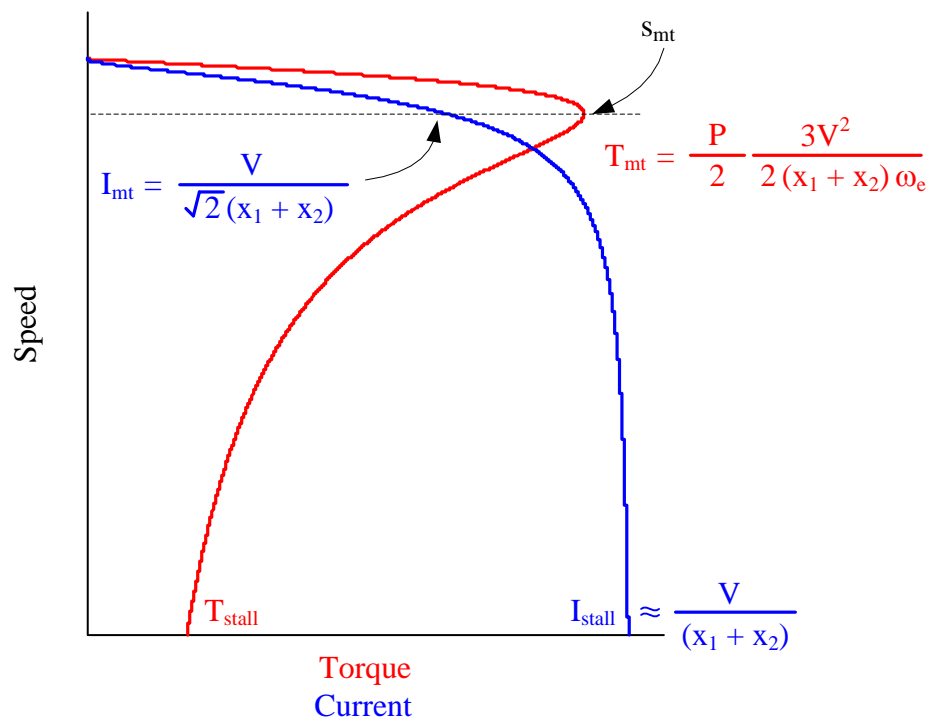
$$P_{ag_mt} = 3I_2^2 \frac{R_2}{s_{mt}} =$$




Speed vs. Torque and Current for Three Phase Induction Motor

Wound Rotor Induction Motor:

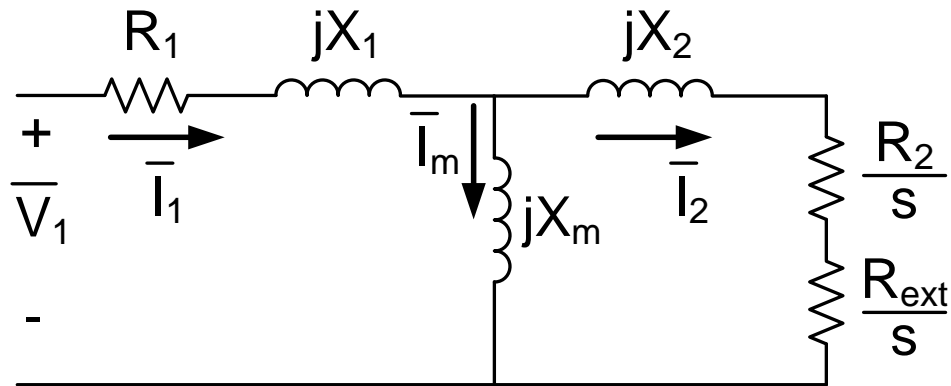

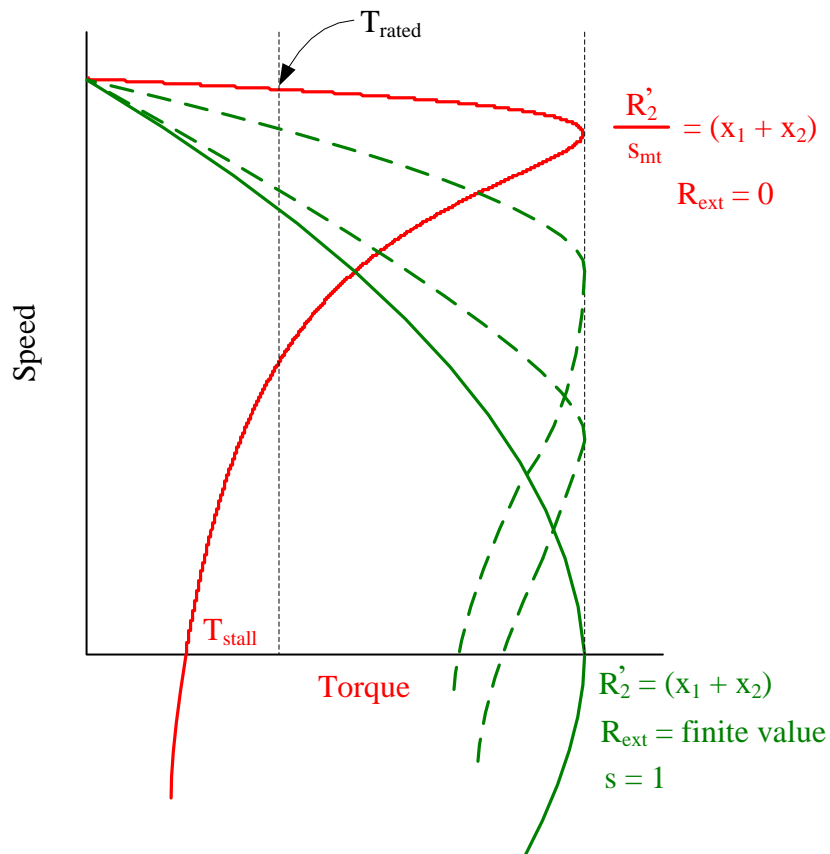Per Phase Equivalent Schematic of Wound Rotor Induction Motor



Speed vs. Torque and Current for Wound Rotor Induction Motor

Exact solution for slip for maximum torque:

Find slip for maximum torque analytically

total impedance

$$z(s) = r_1 + j \cdot x_1 + \frac{\left(\frac{r_2}{s} + j \cdot x_2 \right) \cdot j \cdot x_m}{\frac{r_2}{s} + j \cdot x_2 + j \cdot x_m}$$

stator current

$$I_1(s) = \frac{V_{s_pu}}{r_1 + j \cdot x_1 + \frac{\left(\frac{r_2}{s} + j \cdot x_2 \right) \cdot j \cdot x_m}{\frac{r_2}{s} + j \cdot x_2 + j \cdot x_m}}$$

mutual voltage

$$V_m(s) = V_{s_pu} - \frac{V_{s_pu}}{r_1 + j \cdot x_1 + \frac{\left(\frac{r_2}{s} + j \cdot x_2 \right) \cdot j \cdot x_m}{\frac{r_2}{s} + j \cdot x_2 + j \cdot x_m}} \cdot (r_1 + j \cdot x_1)$$

rotor current

$$I_r(s) = \frac{\frac{V_{s_pu} \cdot s \cdot x_2 \cdot x_m \cdot j^2 + V_{s_pu} \cdot r_2 \cdot x_m \cdot j}{\left(\frac{r_2}{s} + j \cdot x_2 \right)}}{\frac{\left(s \cdot x_1 \cdot x_2 + s \cdot x_1 \cdot x_m + s \cdot x_2 \cdot x_m \right) \cdot j^2 + \left(r_2 \cdot x_1 + r_2 \cdot x_m + r_1 \cdot s \cdot x_2 + r_1 \cdot s \cdot x_m \right) \cdot j + r_1 \cdot r_2}{\left(\frac{r_2}{s} + j \cdot x_2 \right)}} =$$

$$\frac{V_{s_pu} \cdot s \cdot x_m \cdot j}{\left[s \cdot (x_2 + x_m) \cdot r_1 + (x_1 + x_m) \cdot r_2 \right] \cdot j + \left[r_1 \cdot r_2 - \left[(x_1 \cdot x_2 + x_1 \cdot x_m + x_2 \cdot x_m) \cdot s \right] \right]}$$

magnitude of rotor current

$$|I_r| = \sqrt{\frac{(V_{s_pu} \cdot s \cdot x_m)^2}{[s \cdot (x_2 + x_m) \cdot r_1 + (x_1 + x_m) \cdot r_2]^2 + [r_1 \cdot r_2 - [(x_1 \cdot x_2 + x_1 \cdot x_m + x_2 \cdot x_m) \cdot s]]^2}}$$

Torque


$$T_{pu}(s) = \frac{(|I_r|)^2 \cdot r_2}{s \cdot \omega_b} = \frac{\frac{(V_{s_pu} \cdot s \cdot x_m)^2}{[s \cdot (x_2 + x_m) \cdot r_1 + (x_1 + x_m) \cdot r_2]^2 + [r_1 \cdot r_2 - [(x_1 \cdot x_2 + x_1 \cdot x_m + x_2 \cdot x_m) \cdot s]]^2} \cdot r_2}{s \cdot \omega_b}$$

Differentiate torque with respect to slip and set to zero to maximize

$$s_{mt} = \sqrt{\frac{r_1^2 \cdot r_2^2 + r_2^2 \cdot x_1^2 + 2 \cdot r_2^2 \cdot x_1 \cdot x_m + r_2^2 \cdot x_m^2}{r_1^2 \cdot x_2^2 + 2 \cdot r_1^2 \cdot x_2 \cdot x_m + r_1^2 \cdot x_m^2 + x_1^2 \cdot x_2^2 + 2 \cdot x_1^2 \cdot x_2 \cdot x_m + x_1^2 \cdot x_m^2 + 2 \cdot x_1 \cdot x_2^2 \cdot x_m + 2 \cdot x_1 \cdot x_2 \cdot x_m^2 + x_2^2 \cdot x_m^2}}$$

Now, the easy way:

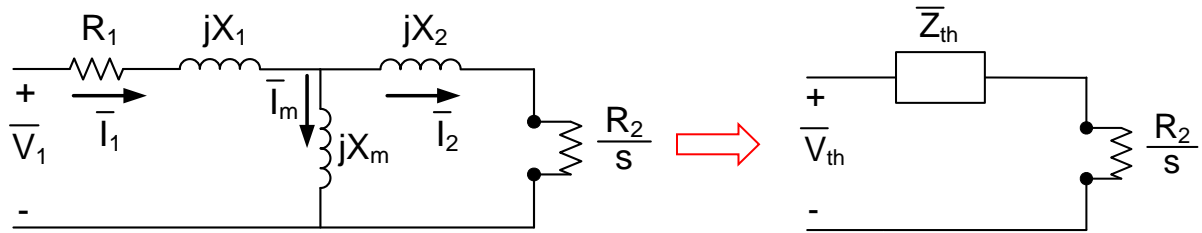Thevenin Equivalent Circuit for a voltage source



Thevenin Equivalent Circuit

$$\bar{Z}_{th} =$$

$$\frac{R_2}{s_{mt}} = |\bar{Z}_{th}| = |jX_2 + jX_m \parallel (R_1 + jX_1)|$$

$$T_{mt} =$$

What's the Thevenin equivalent voltage?

$$\bar{V}_{th} = \bar{V}_1 \frac{jX_m}{R_1 + jX_1 + jX_m}$$

Per Unit Representation of Machines

$$P_b = P_{rated} \quad V_b = V_{\phi_rated} \quad \omega_b = \omega_{e_rated}$$

$$P_b = 3V_b I_b \rightarrow I_b = \frac{P_b}{3V_b} = \frac{P_{rated}}{3V_{\phi_rated}} = \frac{P_{rated}}{\sqrt{3}V_{LL_rated}}$$

$$Z_b = \frac{V_b}{I_b} = \frac{3V_b^2}{P_b} = \frac{V_{LL_rated}^2}{P_b} \quad \omega_{mb} = \frac{\omega_b}{P/2}$$

$$T_b = \frac{P_b}{\omega_{mb}} = \frac{P}{2} \frac{P_{rated}}{\omega_{e_rated}}$$

$$I_{rated} = \frac{\text{input VA}}{V} = \frac{P_{rated}}{\eta \cos \theta \sqrt{3} V_{LL_rated}} =$$

$$T_{rated} = \frac{P}{2} \frac{P_{rated}}{\omega_{r_rated}} = \frac{P}{2} \frac{P_{rated}}{(1-s_{rated})\omega_{e_rated}} =$$

$$\frac{V}{V_b} = \frac{I}{I_b} \frac{Z}{Z_b} \quad \frac{P}{P_b} = \frac{3V_{\phi} V_{\phi} \cos \theta}{3V_b I_b}$$

$$V_{pu} = I_{pu} Z_{pu} \quad P_{pu} = V_{pu} I_{pu} \cos \theta$$


$$\frac{T}{T_b} = \frac{\frac{3}{2} I_2^2 \frac{R_2}{s\omega_e}}{\frac{3}{2} \frac{P}{\omega_{e_rated}} \frac{V_b I_b}{\omega_{e_rated}}} = \frac{\frac{3}{2} I_2^2 \frac{R_2}{s\omega_e}}{\frac{3}{2} \frac{I_b^2 Z_b}{\omega_{e_rated}}} = \frac{I_{pu}^2 R_{pu}}{s\omega_{e_pu}}$$

EE 560 – Electric Machines and Drives


Prof. N.J. Nagel, Autumn 2020 – Lecture 4

for a good motor:


	Large Machines		Small Machines	
$R_1 \rightarrow 0$		$< R_1 <$		pu
$X_m \rightarrow \infty$		$> X_m >$		pu
R_2		$< R_2 <$		pu
X_1, X_2		$< X_1 + X_2 <$		pu

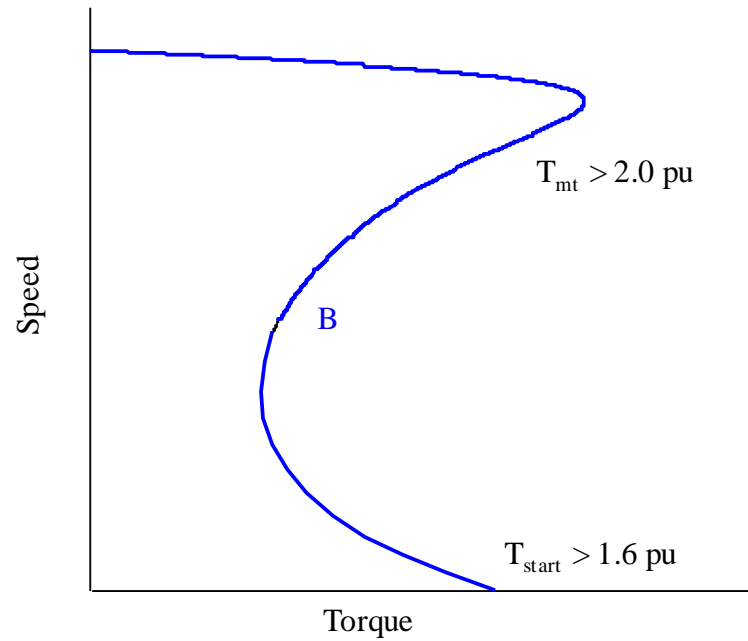

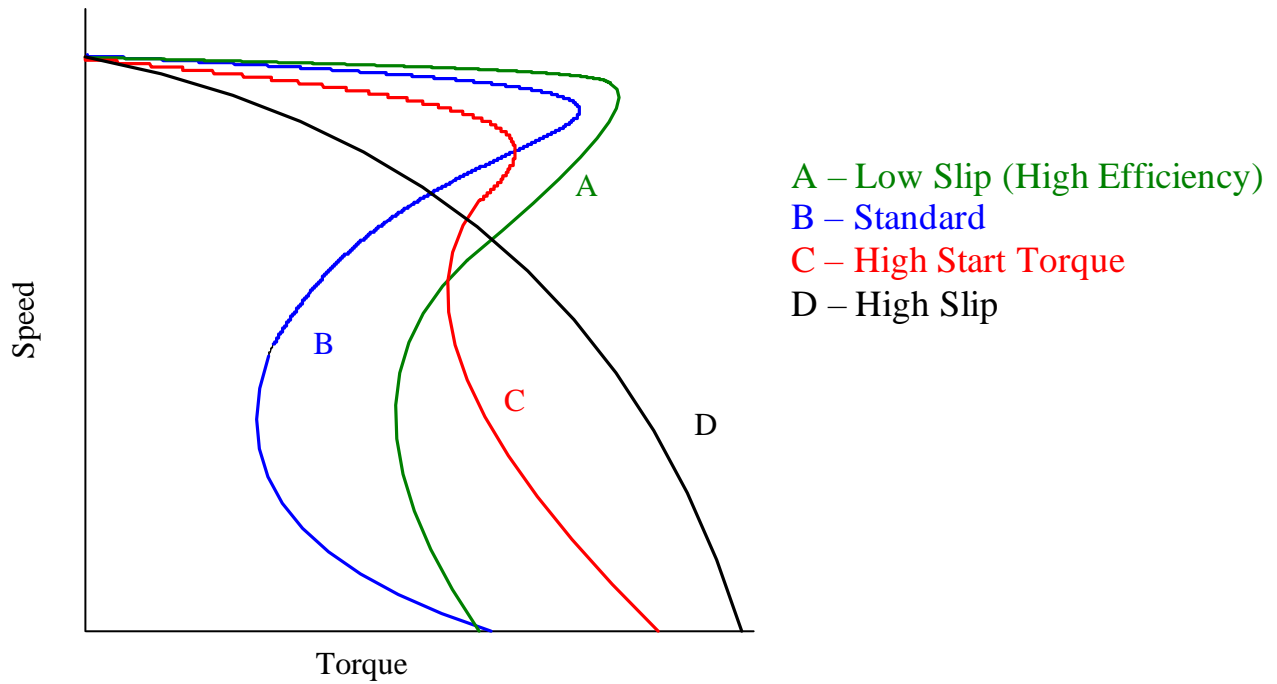Typical pu Speed Torque Curve for a NEMA Class B Induction Motor




NEMA Standard Class Motors

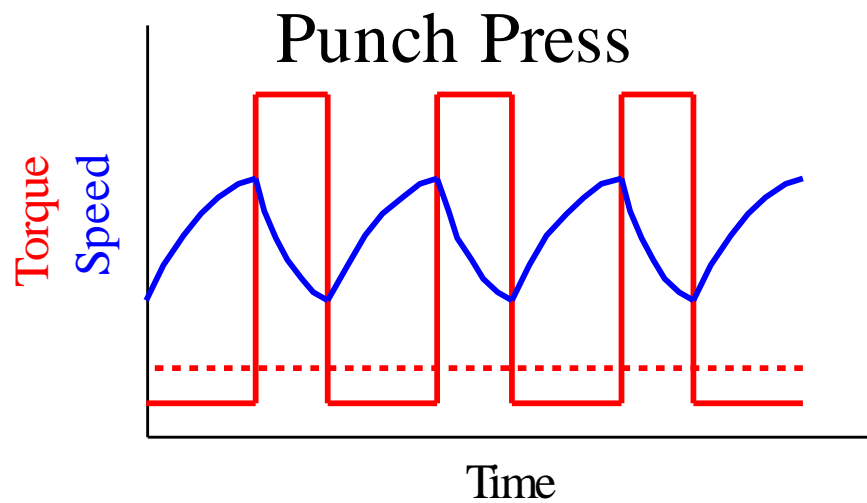

NEMA Class D Typical Application


Induction Motor Parameter Variation:

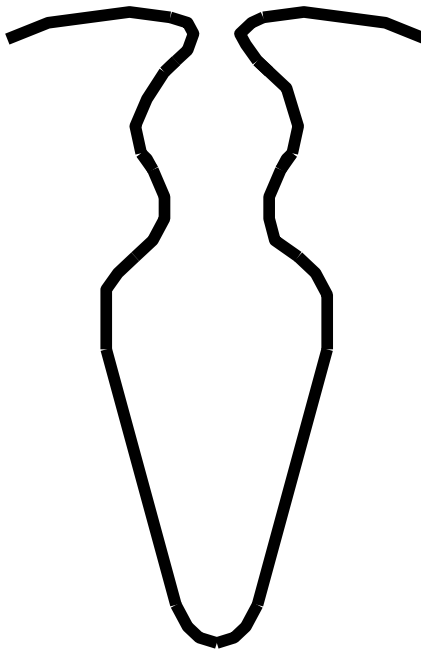- 1) Frequency Effects
 - a. Rotor Slip Frequency Effects
 - i. R increases with frequency (good)
 - ii. L decreases with frequency (partly good)
 - b. Stator Skin Effects (bad)
- 2) Flux Level (Saturation)




Double Cage Induction Motor Rotor Slot


Induction Motor Performance Summary:

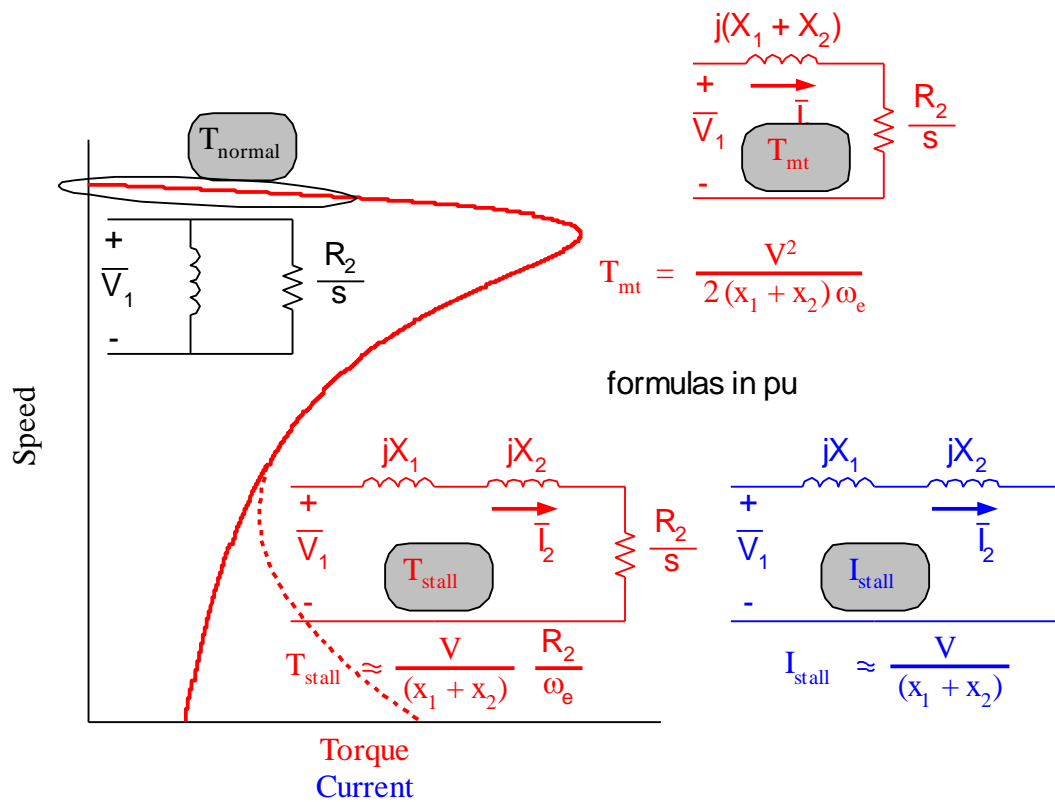

Induction Motor Performance Summary

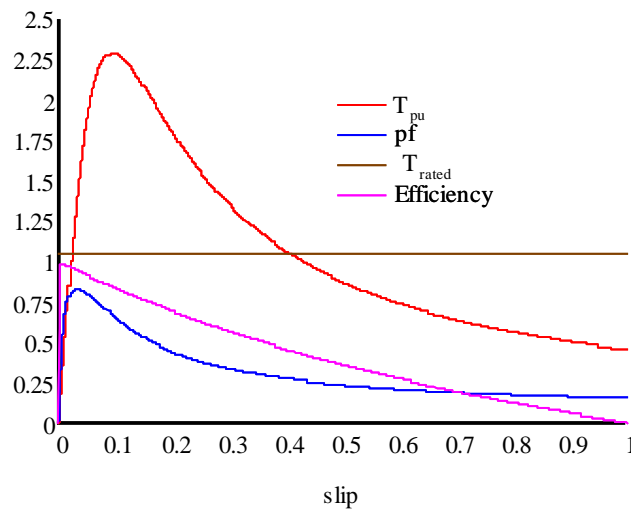

Induction Motor Performance vs. Slip


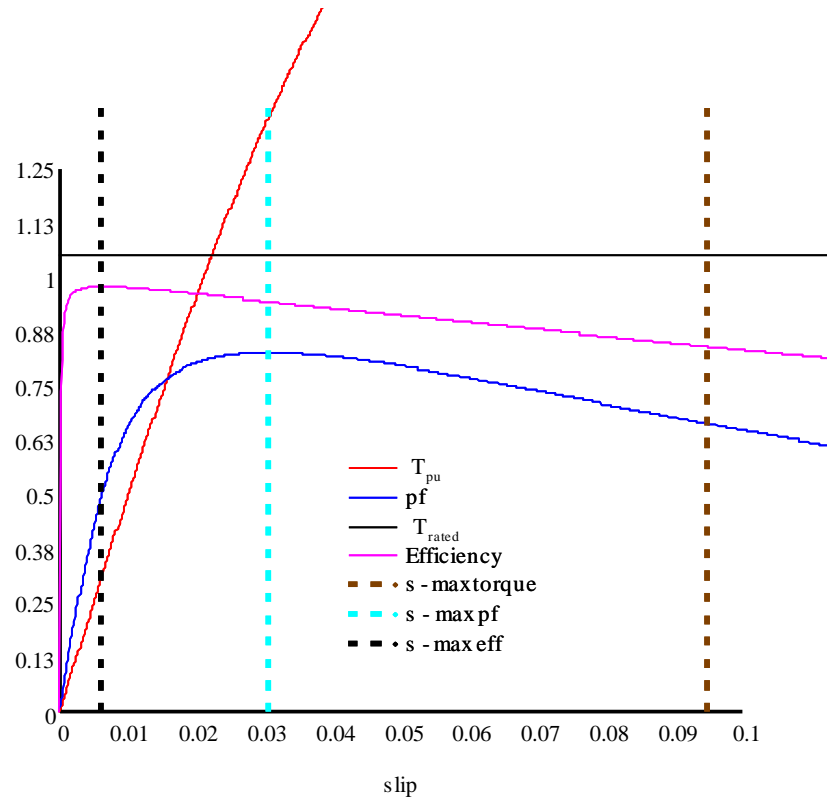


Zoomed-in Induction Motor Performance vs. Slip

Operation of Induction Machine above ω_e (Induction Generator):

EE 560 – Electric Machines and Drives

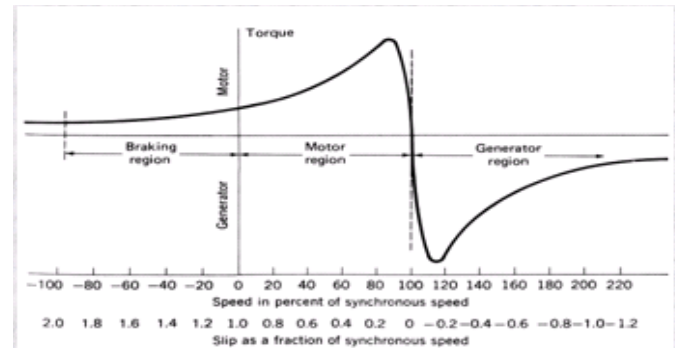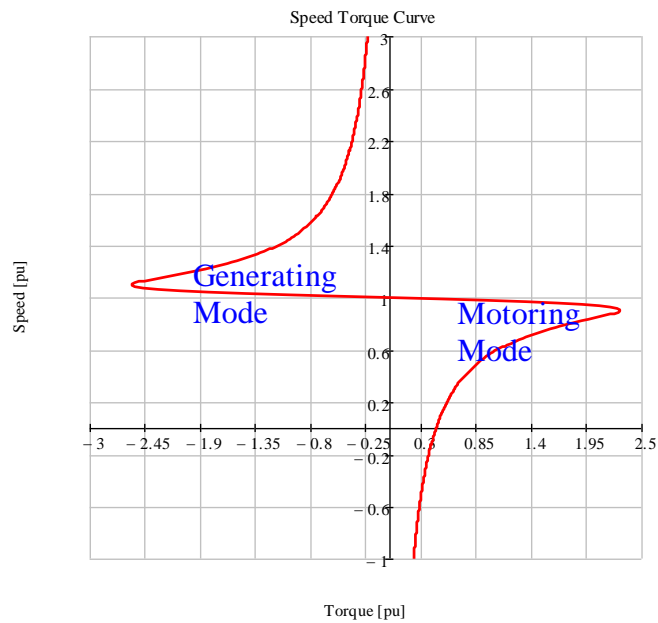Prof. N.J. Nagel, Autumn 2020 – Lecture 4



<http://www.ece.osu.edu/ems/ee743/Lectures/lect24.ppt>